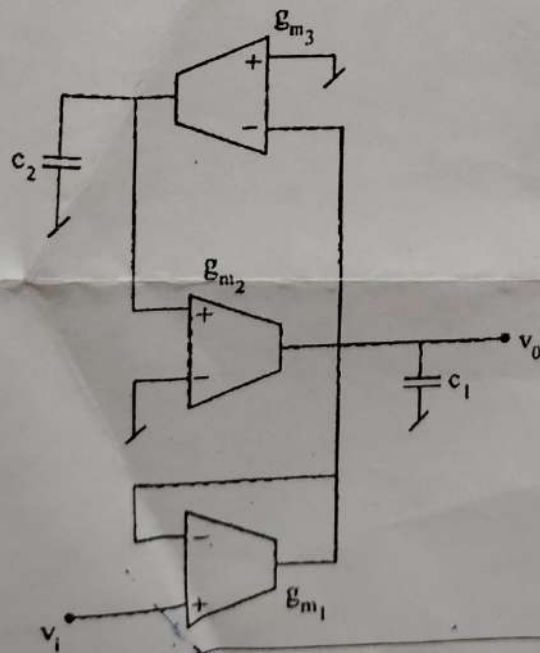


End Term Examination
(CBCS)(SUBJECTIVE TYPE) (Offline)
Course Name: B.Tech. ECE, Semester:4
(May, 2025)

3

Subject Code: BEC 202	Subject: Linear Integrated Circuits (LIC)
Time: 3 Hours	Maximum Marks :60

Note: Q1 is compulsory. Attempt one question each from the Units I, II, III & IV.

Q1	(2.5*8=20)	CO Mapping
a) The output voltage of Op-amp is changes by 20V in 4 μ sec. What is the slew rate of Op-amp?		CO1
b) Explain the virtual ground concept with a suitable example.		CO1
c) What is precision diode? What part it plays in a half wave rectifier?		CO2
d) Explain the basic principle of a RC Phase shift oscillator.		CO2
e) Give limitations of an Operational Transconductance Amplifier (OTA).		CO3
f) Discuss the power conversion efficiency of a Class A Amplifier.		CO3
g) For which applications active filters are preferred over passive filters and why?		CO4
h) What is a phase detector? What are its types?		CO4
UNIT I		
Q2	Explain the meaning of open loop and closed loop operation of an op-amp. Discuss different circuits and their working for both types of operation of Op-Amp.	(10) CO Mapping CO1
Q3	Discuss about the various methods used for improving CMRR of the Op-Amp.	(10) CO1
UNIT II		
Q4	Draw the circuit of a Monostable Multivibrator using Op-Amp. Explain its operation and find out the mathematical expression for pulse width 'T' for the monostable multivibrator.	(10) CO Mapping CO2
Q5	Design an op-amp differentiator that will differentiate an input signal with $f_{max} = 500$ Hz. Draw the output waveform for a sine wave of 2V peak at 200 Hz applied to the differentiator.	(10) CO2
UNIT III		
Q6	Find the transfer function of the circuit given in Figure below:	(10) CO Mapping CO3
		

Q7	Explain the operation of Class A Push-Pull Amplifier. Give circuit diagram and detailed working.	(10)	CO3
UNIT IV			
Q8	Design a fifth order Butterworth low-pass filter having upper cut-off frequency 2kHz.	(10)	CO Mapping CO4
Q9	Write short notes on the following:- (a) Monostable operation of 555 Timer (b) Block schematic of Phase Locked Loop (PLL)	(10)	CO4