

# Indian Institute of Information Technology, Design and Manufacturing Jabalpur

## Quiz-1

Network Theory, Analysis & Synthesis (EC203B)

16-09-2023

Marks: 50

Time: 01:0 HR

Answer all the questions.

Assume missing data (if any)

Q1. Write the expressions for the power dissipation and storage (whichever is applicable) in the resistor, inductor and capacitor. [03]

Q2. Write the expressions for the voltage and currents across the resistor, inductor, capacitor and diode. [06]

Q3. An inductor, Capacitor and Resistor are excited individually with voltage source and connected through a switch. Illustrate.

(a) Currents and voltages at  $t=0^-$ ,  $0^+$  &  $t=\infty$  when switch is closed to  $t=0$  [06]

(b) Currents and voltages at  $t=0^-$ ,  $0^+$  &  $t=\infty$  when switch is closed for a long time and opened  $t=0$  [05]

Q4. What are the applications of Laplace transform and how it is different from the Fourier Transform, explain briefly. [04]

Q5. What are the ideal voltage and current sources, briefly explain? [04]

Q6. An equation of current of RL network is expressed by  $10e^{-2t}$  and it is excited with 20Volts source.

(a) Draw RL network with an appropriate switching position. [03]

(b) Find the values of RL elements and time constant. [04]

Q7. Write the current response for RC circuit for Voltage source excitation connected through a switch at  $t=0$ . [04]

Q8. Draw a frequency spectrum of time domain impulse function. [02]

Q9. Write the dual quantities for capacitor and inductor in tabular form. [04]

Q10. Draw the equivalent circuits of series and shunt RLC network at resonance frequency. [04]

Handwritten notes and equations:

$$i_{\infty} = (i_{\infty} - i_{0+})e^{-\frac{t}{\tau}}$$

$$v_R = \left(\frac{v}{R} - 0\right)e^{-\frac{t}{\tau}}$$

$$\frac{1}{R}(1 - e^{-\frac{t}{\tau}})$$



**Indian Institute of Information Technology, Design and Manufacturing Jabalpur**  
Mid-Sem Exam

**Network Theory (Analysis & Synthesis)-EC203B**

**23-09-2023**

**Marks: 75**


**Time: 02:0 HRS**

**Answer all the questions.**


**Assume missing data (if any)**

**Q1.** Find the voltages  $V_A$ ,  $V_B$ , and  $V_x$  in the network in Fig. (A) using node analysis. **[20]**

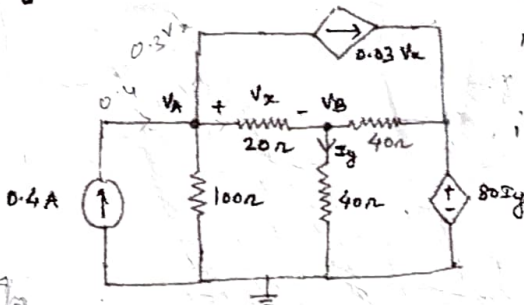**Q2.** Find the currents  $i_1$ ,  $i_2$ , and  $i_3$  in the network in Fig. (B) using mesh analysis. **[15]**




(A)

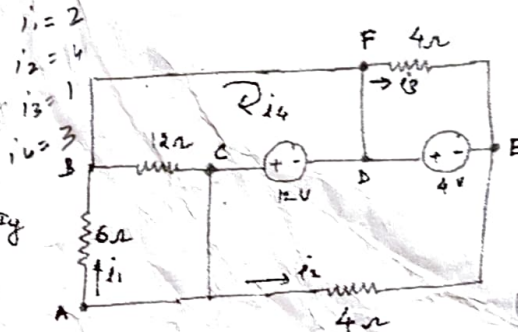


(B)

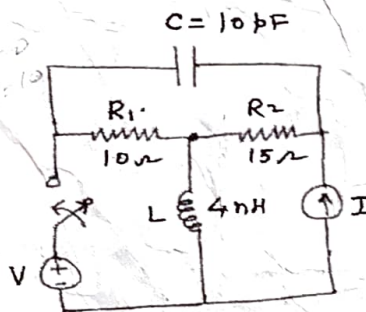**Q3.** Using duality concept convert the network in Fig. (C) into its dual counterpart network and find the values of new elements. **[15]**



(C)

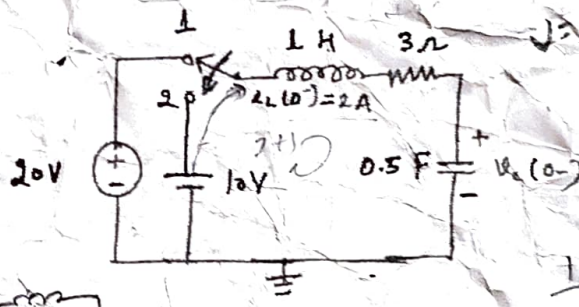

(D)

**Q4.** Using Laplace transform find the current in the loop in Fig. (D) if the switch is moved from contact 1 to 2 at  $t=0$  and before this  $i_L(0^-) = 2A$  and  $v_C(0^-) = 2V$ . **[15]**

**Q5.** Write and explain the below properties of the Laplace transform? **[10]**

(a) Time differentiation (b) Time integration (c) Frequency Shifting (d) Time shifting (d) Time scaling.

$$A(s+2) + B(s+1) = 10$$

$$\frac{A}{(s+1)} + \frac{B}{(s+2)} = \frac{1}{(s+1)(s+2)}$$

$$A(s+2) + B(s+1) = 1$$

$$As + 2A + Bs + B = 1$$

$$As + Bs = 0$$

$$A + B = 0 \quad (i)$$

$$2A + B = 10 \quad (ii)$$

$$A = -B$$

$$-2B + B = 10$$

$$B = -10$$

$$\frac{10}{(s+1)} - \frac{10}{(s+2)}$$

$$10s + 20 - 10s - 10$$

$$A + B = 0$$

$$A - 10 = 0$$

$$A = 10$$