

Roll No.

Total Pages : 4

013102

December 2024

B. Tech. (First Semester)

Basic Electrical Technology (ESC-101A)

Time : 3 Hours]

[Maximum Marks : 75

Note : It is compulsory to answer all the questions (1.5 marks each) of Part A in short. Answer any *four* questions from Part B in detail. Different sub-parts of a question are to be attempted adjacent to each other.

Part A

1. (a) Differentiate the dependent and independent sources. **1.5**
- (b) Distinguish between a current source and voltage source. **1.5**
- (c) Define Apparent power and Power factor. **1.5**
- (d) Define Phase and Phase difference. **1.5**
- (e) Define Earthing. **1.5**
- (f) What is the main purpose of commutator in a DC machine ? **1.5**

- (g) List the advantage of three phase system over a single-phase system. 1.5
- (h) Write the current and voltage relations for delta connected three phase system. 1.5
- (i) List the five house hold application of single-phase induction motor. 1.5
- (j) List the components of a switchgear system. 1.5

Part B

2. (a) In the figure 1 given below $V = 10V$, $R_1 = 10\Omega$, $R_2 = 10\Omega$, $R_3 = 15\Omega$, $R_4 = 20\Omega$ and $R_5 = 5\Omega$. The internal resistance of voltage source is 1Ω . Find the current following through R_5 using Thevenin theorem. 9

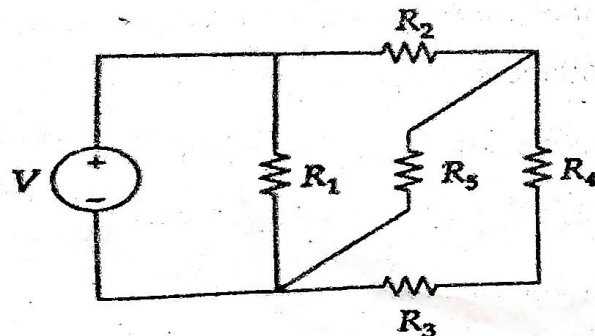


Figure1

- (b) State and prove the Maximum power transfer theorem with suitable example. 6
3. (a) Describe the construction of an induction motor with neat diagrams. 7.5
- (b) Draw and explain the two-wattmeter method of power measurement in a three-phase circuit. 7.5
4. (a) An a. c. series circuit consisting of a pure resistance of 250Ω , inductance of $0.15H$ and capacitance of $80\mu F$ is supplied from a $230V$, $50Hz$. Find : 8
- impedance of the circuit,
 - the current,
 - power drawn by the circuit and
 - the power factor.
- (b) With a neat circuit diagram Explain the construction and principle of operation of DC Motor. 7
5. (a) Define the term resonance. What the conditions for parallel resonance occurrence ?

Derive the expression for parallel resonance frequency and also draw the resonance curve for the same. 8

(b) Draw and explain the working of ELCB. 7

6. (a) A three-phase star connected load consists of three identical inductive coils of resistance 20Ω and inductance $0.5H$. The supply voltage is $400V$, 50 Hz . Calculate : 8

(i) phase current

(ii) line current

(iii) power factor

(iv) total power consumed.

(b) Discuss the different method of power factor improvements. 7

7. Discuss the working of transformer and draw the phasor diagram of transformer for inductive load. Also draw and explain the equivalent circuit of single-phase transformer. 15