

## Basic Electrical Technology (ESC101A)

### Assignment-1 (DC Circuit)

**Problem-1** - Using nodal analysis, find the current flowing in the battery in Fig1.

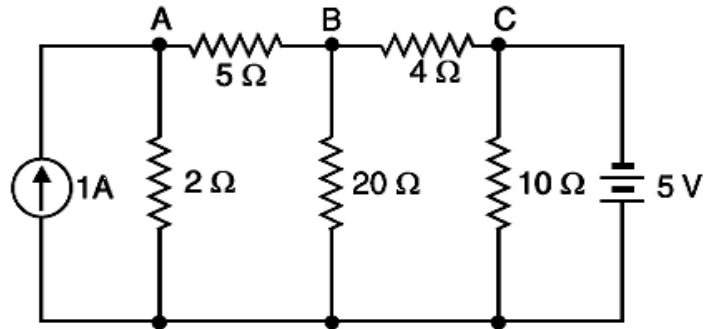


Fig-1

**Problem-2**- Determine Current in each branch using nodal analysis for the given circuit Fig-2

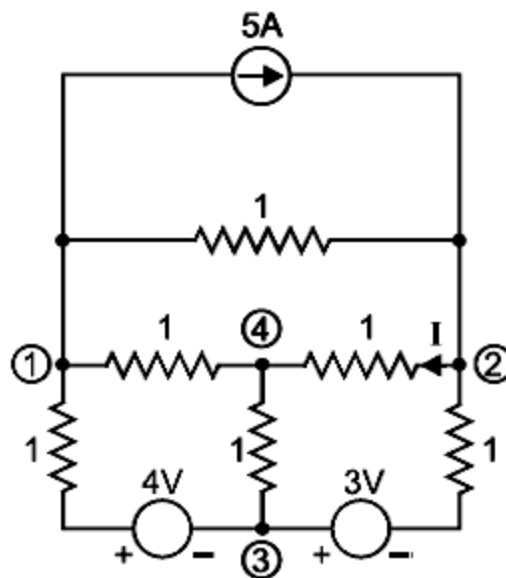


Fig-2

**Problem-3**- Using Mesh Analysis find current in each branch of the given circuit fig-3

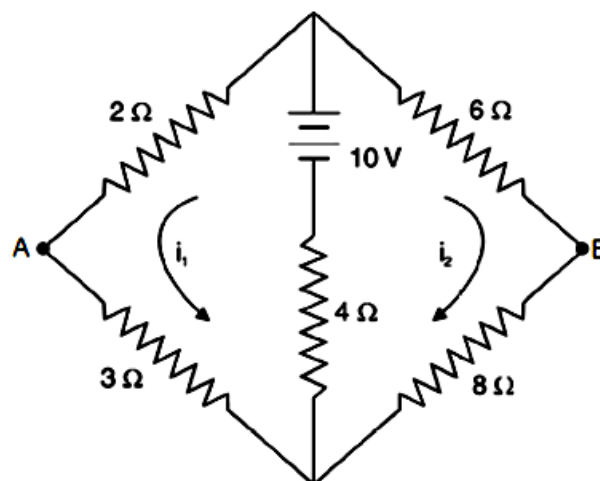


Fig-3

**Problem-4-** By using mesh resistance matrix, calculate the current in each branch of the circuit shown in Fig. 4

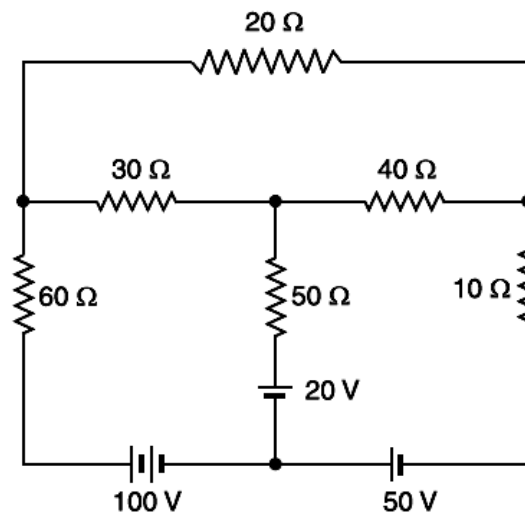


Fig-4

**Problem-5-** Determine the current through 6 ohm resistor using node analysis and mesh analysis.

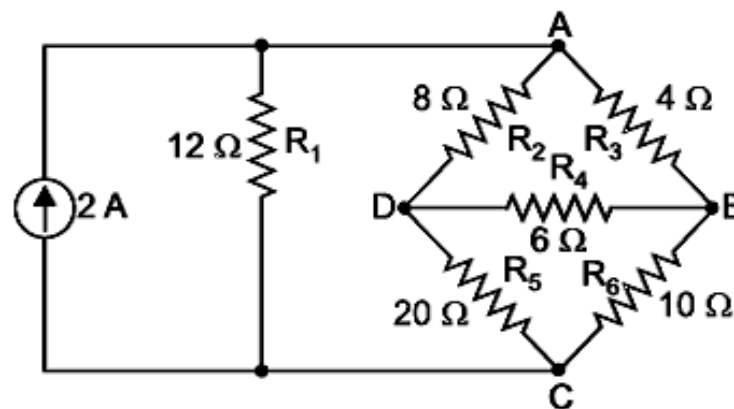


Fig-5

**Problem-6-** Using superposition theorem, find the current through the 40 Ω resistor in the circuit shown in Fig. 6. All resistances are in ohms.

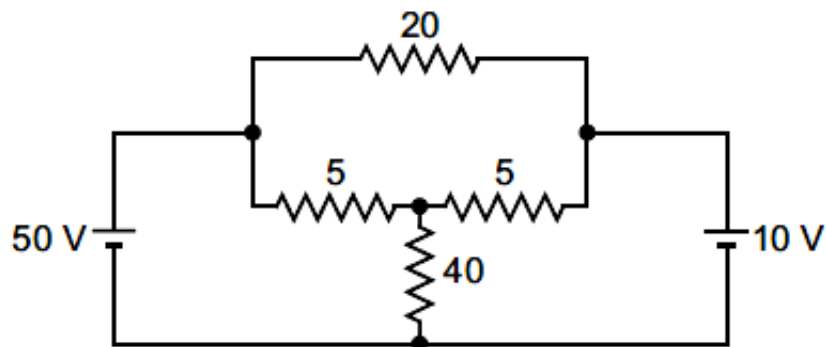


Fig-6

**Problem-7-** Draw the Thevenin's equivalent circuit and find the current through resistance R connected between points a and b in Fig. 7.

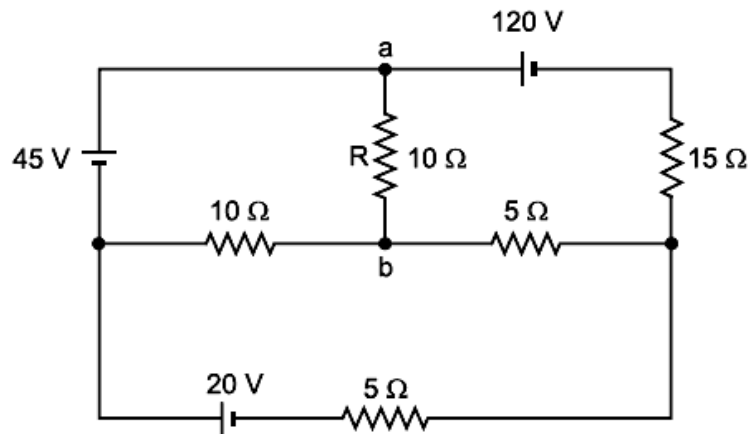


Fig-7

**Problem-8-** A Wheatstone bridge ABCD has the following details :  $AB = 10\ \Omega$ ,  $BC = 30\ \Omega$ ,  $CD = 15\ \Omega$  and  $DA = 20\ \Omega$ . A battery of e.m.f. 2 V and negligible resistance is connected between A and C with A positive. A galvanometer of  $40\ \Omega$  resistance is connected between B and D. Using Thevenin's theorem, determine the magnitude and direction of current in the galvanometer.

**Problem-9-** Draw the Thevenin's and Norton's equivalent circuit for fig-9. Also, determine the current in  $1\ \Omega$  resistor across AB of the network shown in Fig 9. All resistances are in ohms.

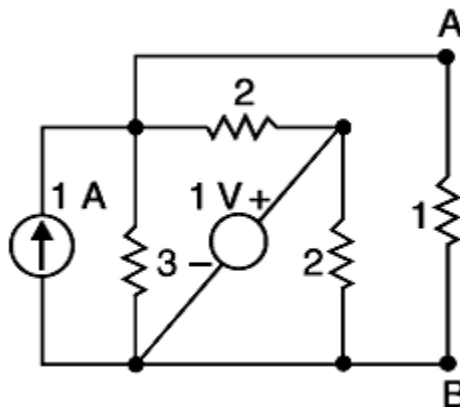


Fig-9

**Problem-10-** For the circuit shown in Fig. 10, find the value of R that will receive maximum power. Determine maximum power.

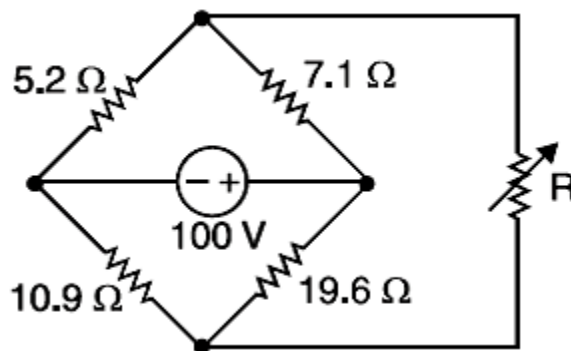


Fig-10

**Problem-11-** Solve the circuit shown in Fig. 11 using nodal analysis.

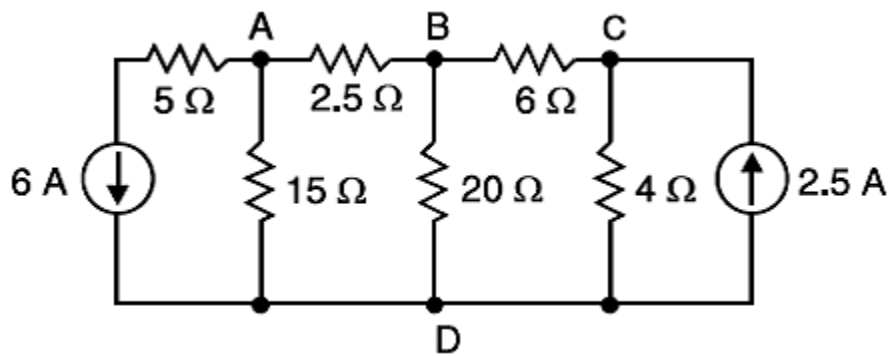


Fig-11

**Problem-12-** Using superposition theorem, find the current in 23 Ω resistor in the circuit shown in Fig. 12

