

School of Electronics Engineering
KIIT UNIVERSITY
BASIC ELECTRONICS (EC-1001)
MID-SEMESTER EXAMINATION

Full Marks: 30

Time: 90 minutes

The figures in the margin indicate full marks.
Candidates are required to give their answers in their own words as far as
Practicable and of all parts of a question at one place only.
Answer any FIVE question including question No.1 which is compulsory.

1. **[2×5]**



- (a) In an extrinsic semiconductor concentration of holes is $5.2 \times 10^{10} \text{ cm}^{-3}$. Calculate concentration of electrons. Intrinsic concentration = $2.3 \times 10^{13} \text{ cm}^{-3}$ at 300K.
- (b) Write down the diode current equation and define each variable.
- (c) What is the effect of temperature on the conductivity of semiconductor and conductor?
- (d) Write down two difference and two similarity between center tap and full wave bridge rectifier
- (e) Differentiate between zener diode and rectifying diode.

2.

- a) Classify the materials on the basis of energy band diagram with proper description. **[3]**
- b) Explain Drift and Diffusion current with proper diagram. **[2]**

3.

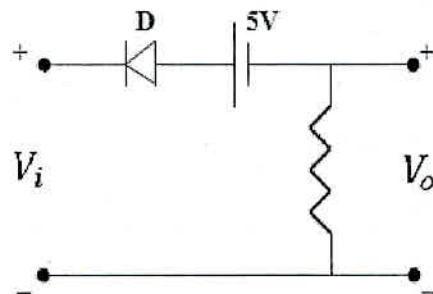
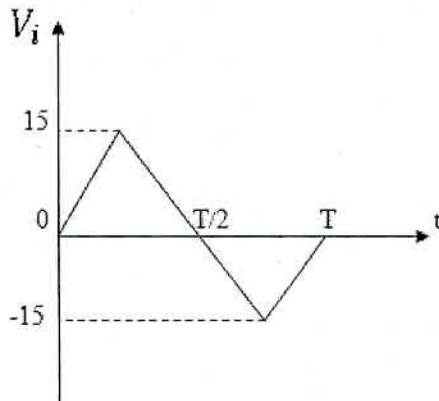
- a) Draw and explain the output waveform for the circuit shown below. (Assume diode D is ideal diode). **[3]**



- b) What do you mean by depletion layer in junction diode and write down the effect of biasing on it? **[2]**

4.

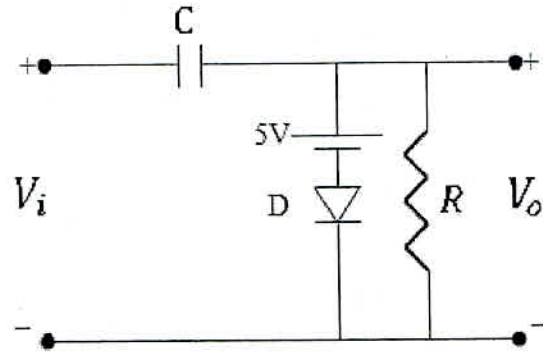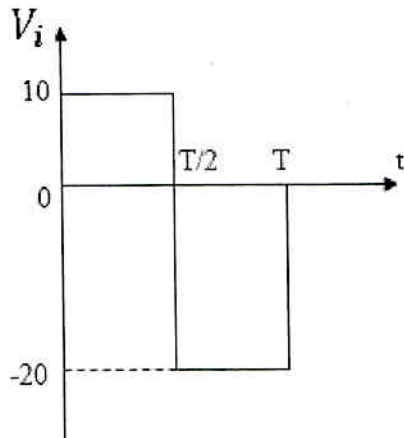- a) Draw and explain the output waveform for the circuit shown below. (Assume diode D is ideal diode). [3]



- b) Differentiate between LED and Photodiode. [2]

5.

- a) With proper diagram explain the operation of bridge full wave rectifier. Also find its efficiency and ripple factor. [3]
 b) What do you mean by equivalent circuit. Briefly explain the diode equivalent circuit. [2]

6.

- a) Explain the operation of Zener diode as a voltage regulator. [3]
 b) Define the static and dynamic resistance of p-n diode. [2]

7. A center tap full wave rectifier uses two diodes with an equivalent forward resistance 50Ω . If the input ac Voltage is $50 \sin(200\pi t)$ and the load resistance of 950Ω . [5]

Determine:

- (i) Peak, avg. and rms value of current
 (ii) Efficiency
 (iii) Ripple factor of the rectifier.

*****ALL THE BEST*****