

National Institute of Technology, Kurukshetra
End Semester Exams (Theory) May/June 2024

Programme: B. Tech, ECE
Subject Code: ECPC-101
Time: Three Hours

Semester: II
Subject Name: Circuit Theory
Max. Marks: 50

Instructions:

1. All the questions are compulsory. Internal choice as applicable
2. All parts of a question must be done at one place.
3. Unless stated otherwise, the symbols have their usual meanings in context with the subject
4. Assume suitable data, if required.

Q. No. 1 Attempt any four

4*2.5

- (a) State and explain substitution theorem with the help of proper circuit diagram
- (b) State and explain KVL and KCL.
- (c) Write down the restrictions on pole and zero locations for Driving Point Function
- (d) Derive the expression for star-delta conversion.
- (e) Derive the expression of Quality factor in series RLC circuit
- (f) State and explain initial and final value theorem in Laplace transform

Q. No. 2

2*5

- (a) Find the voltage V in the network shown in Fig. 1 which makes the current in the 10Ω resistor zero.

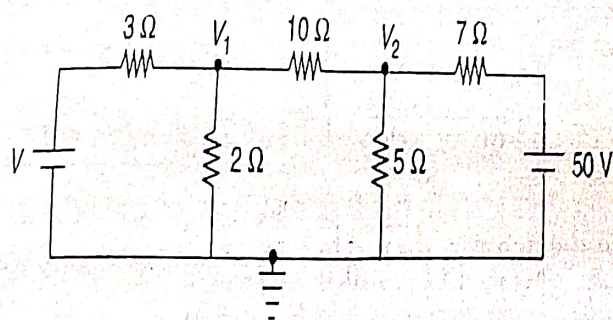


Fig. 1

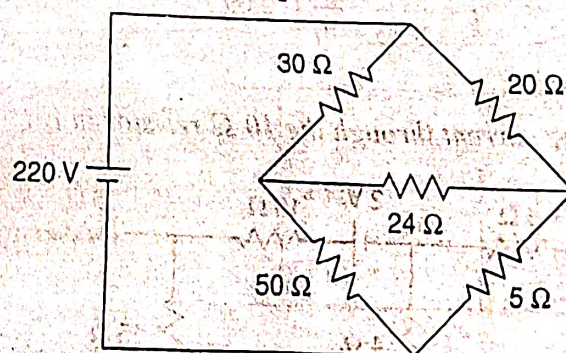


Fig. 2

- (b) Determine the current through the 24Ω resistor in Fig. 2 using thevenin's theorem

Q. No. 3

2*5

- (a) Derive the expression for the resonant frequency of the parallel circuit as shown in Fig. 3
- (b) In the network shown in Fig. 4, a steady state is reached with switch open. At $t=0$, the switch is closed. Find the three loop currents at $t=0^+$.

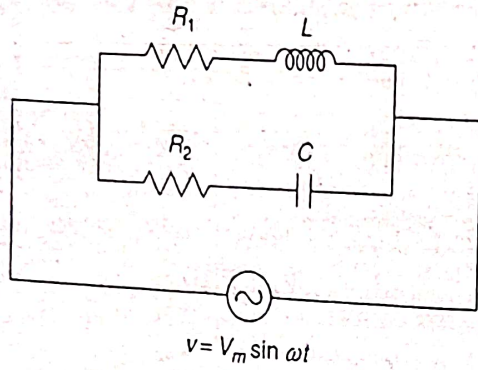


Fig. 3

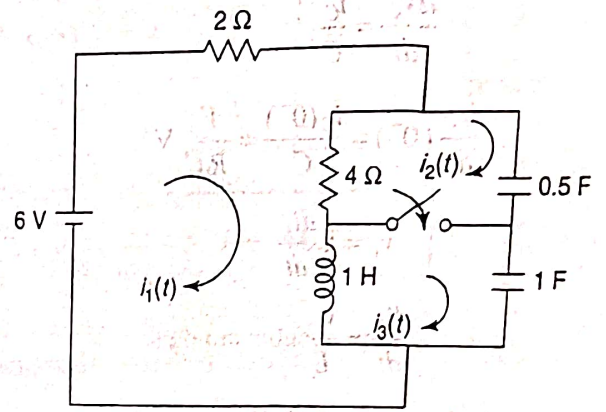


Fig. 4

Q. No. 4

- (a) In the network given in Fig. 5, the switch is closed at $t=0$ with the network previously unenergised (zero initial conditions). Determine current $i_1(t)$. 2*5
- (b) Find the network function $\frac{V_2}{V_1}$ for the network shown in Fig. 6.

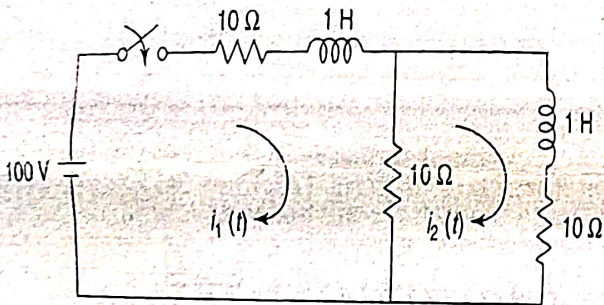


Fig. 5

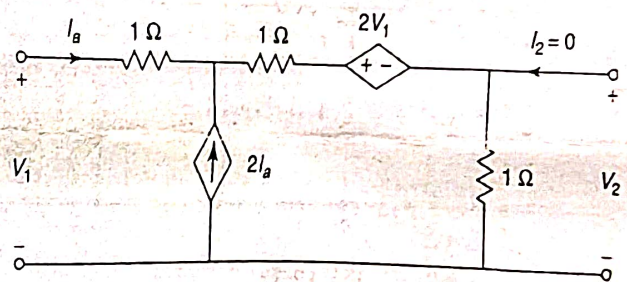


Fig. 6

Q. No. 5

- (a) A network is shown in Fig. 7. The poles and zeros of the driving point function $Z(s)$ of this network are at the following places: 2*5
Poles at $-\frac{1}{2} \pm j\frac{\sqrt{3}}{2}$ and Zero at -1 . If $Z(j0)=1$, find the value of R , L and C .
- (b) For the network shown in Fig. 8, find the h parameters.

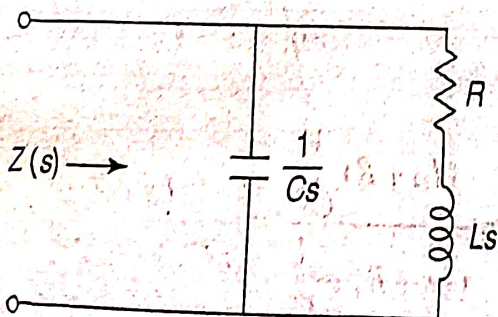


Fig. 7

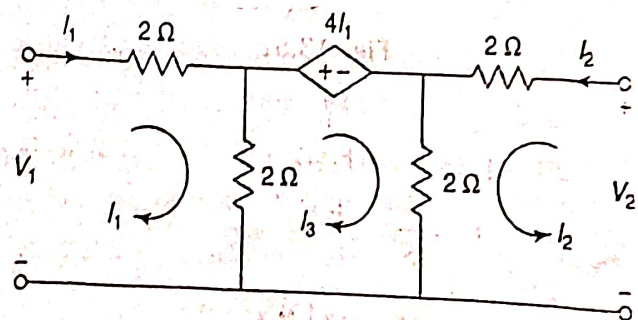


Fig. 8