



PDPM-Indian Institute of Information Technology,
Design and Manufacturing Jabalpur
Electronics Devices and Circuits (Code: EC204a)

Time: 2 Hours

Mid-Term, Sep. 21, 2023

Maximum Marks: 30

1. What is the concentration of holes in Si crystals having donor concentration of $1.4 \times 10^{24}/\text{cm}^3$ when the intrinsic carrier concentration is $1.4 \times 10^{18}/\text{cm}^3$? Find the ratio of electron to hole concentration. [2]
2. A silicon diode has reverse saturation current of $2.5 \mu\text{A}$ at 3000K . Find the forward voltage for a forward current of 10 mA . You may use $V_T = 26 \text{ mV}$. [2]
3. How does the reverse saturation current of a $p-n$ diode vary with temperature? How does the diode voltage (at a constant current) vary with temperature? Calculate the anticipated factor by which the reverse saturation current of a germanium diode is multiplied when the temperature is increased from 25 to 80°C . [1, 1, 2]
4. Describe the physical mechanism for Zener breakdown. [2]
5. Explain base-width modulation (the early effect) with the aid of plot of potential throughout the base region. [2]
6. A BJT has $\alpha = 0.99$, $I_B = 25 \mu\text{A}$, and $I_{CBO} = 200 \text{ nA}$. Find I_C and I_E . [2]
7. Analyze the circuit given in Fig.1 to determine all the node voltages and branch currents. Assume $\beta = 100$. [5]
8. If the Si transistor used in the circuit of Fig.2 has a minimum value of $\beta = 30$ and $I_{CBO} = 10 \text{ nA}$ at 25°C . If $R_1 = 15\text{K}$ and $V_i = 1 \text{ V}$, find V_o and show that Q is cutoff. [5]
9. The CE transistor used in the circuit of Fig.3 has $\beta = 100$. Voltage and current conventions are the same as discussed in the class.
 - a) Find V_{BB} if $V_{CC} = 10 \text{ V}$, $V_{CE} = -1 \text{ V}$, and $R_L = 250\Omega$.
 - b) If $V_{CC} = 10 \text{ V}$, find R_L so that $I_C = -20 \text{ mA}$ and $V_{CE} = -4 \text{ V}$. Find V_{BB} .

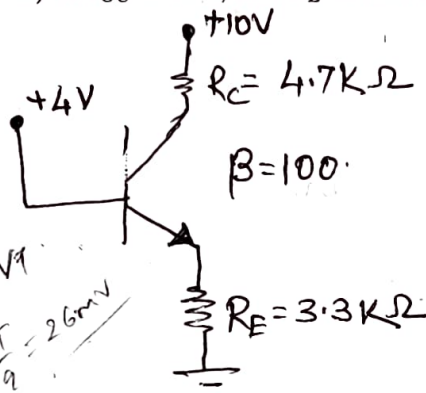


Fig. 1 (Q.7)

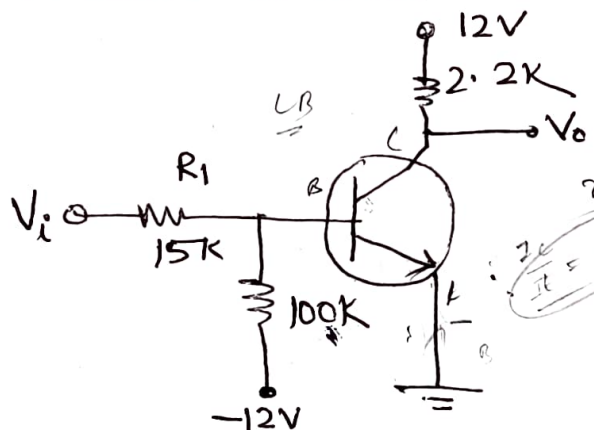


Fig. 2 (Q.8)

Student's name: Prateek Pandey

End of exam

P.T.O.

$$I_B + I_C = I_E \quad (i)$$

$$I_C = \alpha I_E + I_{CBO} \quad (ii)$$

$$\alpha = \frac{I_C}{I_E}$$

$$\beta = \frac{I_C}{I_B}$$

$$I_B + I_C = I_E$$

$$1 + \beta = \frac{I_C}{I_B} \quad (i)$$

$$\frac{I_B}{I_E} = 1 - \alpha \quad (ii)$$

$$1 + \beta = \frac{1}{1 - \alpha}$$

$$\beta = \frac{1}{1 - \alpha}$$

$$\frac{1 - (1 - \alpha)}{1 - \alpha}$$

$$\frac{\alpha}{1 - \alpha} = \beta$$


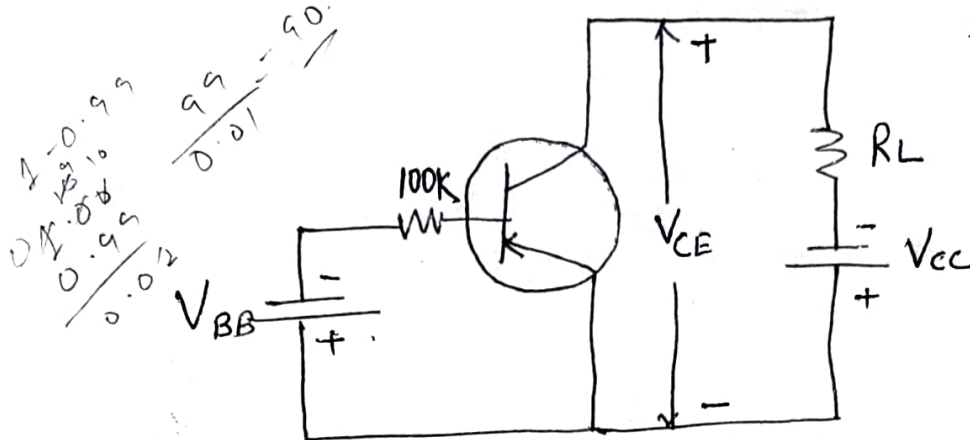




Fig-3 (Q.9)

$$V_{BE} - I_E R_E = 0$$

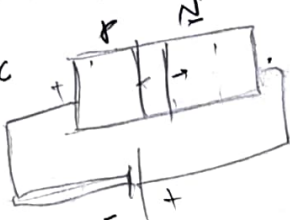

$$\beta = \frac{I_C}{I_B} = \frac{1 - \alpha}{\alpha} \Rightarrow \alpha = \frac{\beta}{\beta + 1}$$
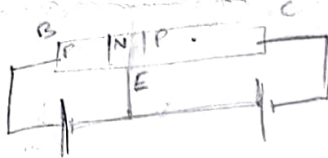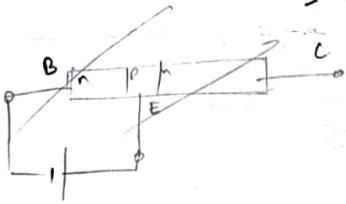
$$\frac{I_C}{I_E} = \frac{I_B}{I_E} = \beta$$



$$1 + \beta = \frac{I_E}{I_B}$$

$$I_B + I_C = I_E$$

$$A' \times B' \times C'$$



$$1 + \beta = \frac{I_E}{I_B}$$


$$\frac{1}{1 + \beta} = 1 - \alpha$$

$$\alpha = \frac{1 + \beta - 1}{1 + \beta}$$


$$I_C \times I_B = I_E$$

$$1 - \frac{1}{1 + \beta}$$

$$\frac{1 - \alpha - 1}{1 - \alpha}$$

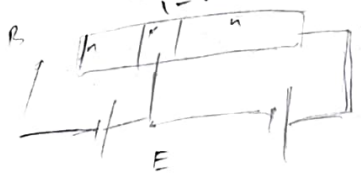

$$\frac{I_C}{I_B} = \beta$$

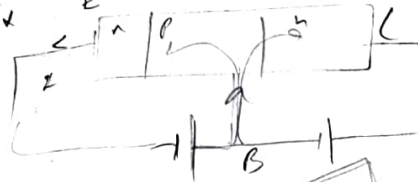


$$I_B + I_C = I_E$$

$$I_B + I_C = I_E$$

$$I_E = \alpha I_B + I_{CBO}$$

$$\frac{I_C}{I_E} = \alpha$$

$$\alpha = \frac{\beta}{1 + \beta}$$

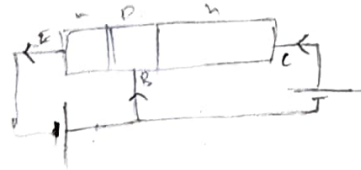

$$I_C = \alpha I_E - I_{CBO}$$



PDPM-Indian Institute of Information Technology,
Design and Manufacturing Jabalpur
Electronics Devices and Circuits (Code: EC204a)


PART-B-

Time: 2 Hours

End-Term, Nov. 24, 2023

Maximum Marks: 70

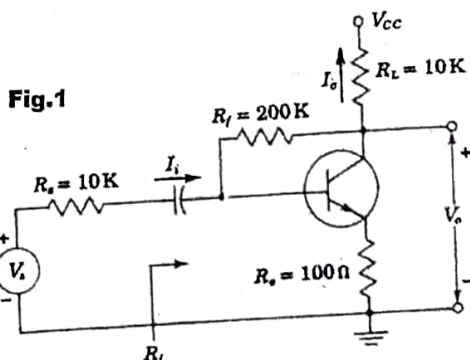1. Draw a family of common source drain characteristics for an n-channel JFET. Explain the shape of these curves qualitatively. [10]
2. Define the pinch-off voltage of a JFET. Sketch the depletion region before and after pinch-off. [6]
3. Sketch and discuss the cross section of a p-channel enhancement MOSFET. Draw two circuit symbols for this MOSFET. [6]
4. Draw a fixed biased circuit. Explain why the circuit is unsatisfactory if the transistor is replaced by another of the same type? [3,3]
5. For the circuit shown in Fig.1, calculate $A_I = I_o/I_i$, A_V , A_{V_s} , and $R - i$. Given $h_{ie} = 1100\Omega$, $h_{re} = 2.5 \times 10^{-4}$, $h_{fe} = 50$, and $1/h_{oe} = 40K$.



6. Draw and explain a circuit which uses a diode to compensate for changes (a) in V_{BE} and (b) in I_{CO} . [15]
7. A silicon transistor with $V_{BE,sat} = 0.8V$, $\beta = 100$, $V_{CE,sat} = 0.2V$ is used in circuit of Fig.2. Find the minimum value of R_c for which the transistor remains in saturation. [7]

Student's name:

Please go on to the next page...

$$21 \times 10^{-6} \text{ A} \times 100 = 2.1 \text{ mA}$$

$$21 \times 10^{-6} \text{ A} = 2.1 \text{ mA}$$

$$V_{CE} = I_C R_C + 10$$

$$0.2 = I_C R_C + 10$$

$$I_B = 21 \mu\text{A}$$

$$\beta = \frac{I_C}{I_B}$$

E B C
1 2 3


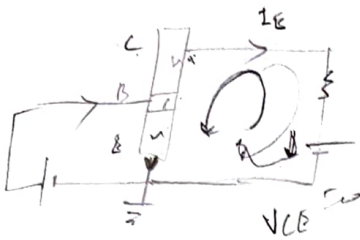


Fig. 2

$$-10 + V_{CE} - I_C R_C = 0$$

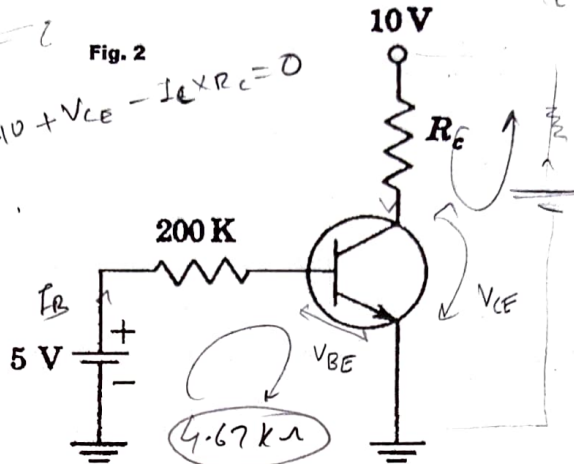

$$10 - I_C R_C = 0$$

$$V_{CE} + I_C R_C = 10$$

$$5 - I_B R_E - V_{BE} = 0$$


$$5 = V_{BE} + I_B \times 200\text{K}$$

$$5 - 0.8 = I_B \times 200\text{K}$$

$$0.021 \text{ mA} = I_B$$

8. For the circuit shown in Fig.3, assume $\beta = 100$. Find if the silicon transistor is in cutoff, saturation or in the active region. Find V_o .

Fig.3

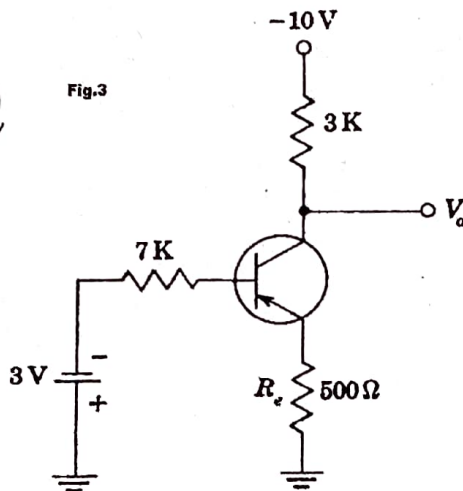

J ₁	J ₂	
f.B	R.B	active
F.B	F.B	ON state
R.B	R.B	01 work
R.B	F.B	→ 50

[10]