

Sr. No. DD2204

August/September 2022

B.Tech - II SEMESTER

Basic Electrical Technology (ESC-101-A)

Time: 3 Hours

Max. Marks: 75

Instructions:


1. It is compulsory to answer all the questions (1.5 marks each) of Part -A in short.
2. Answer any four questions from Part -B in detail.
3. Different sub-parts of a question are to be attempted adjacent to each other.
4. Any other specific instructions

PART -A

- Q1 (a) Enumerate various limitations of ohms law. (1.5)[C01]
- (b) Convert 4A source with its parallel resistance of  $15\Omega$  into its equivalent voltage source. (1.5)[C01]
- (c) Differentiate between active and passive components. (1.5)[C01]
- (d) Define dynamic impedance. Also write its unit. (1.5)[C02]
- (e) Explain why a series resonance is called voltage resonance. (1.5)[C02]
- (f) List various applications of autotransformer. (1.5)[C03]
- (g) In case of power measurement by two-wattmeter method for 3-phase balanced load, under what conditions: the one wattmeter will give zero reading and whole of the power will be measured by the other wattmeter. (1.5)[C02]
- (h) List various methods of starting a single-phase Induction motor. (1.5)[C03]
- (i) What is the function of commutator in dc machines? (1.5)[C03]
- (j) Why earthing is provided? (1.5)[C04]

PART -B

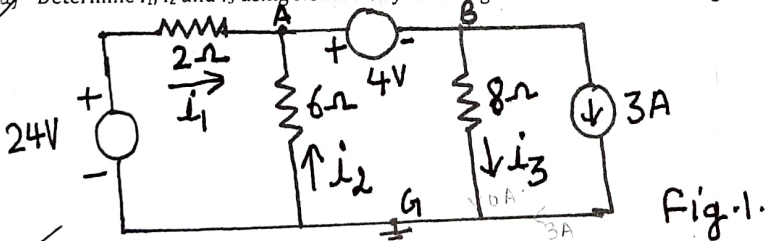- Q2 (a) Determine  $i_1$ ,  $i_2$  and  $i_3$  using Nodal analysis for a given circuit shown in Fig.1. (8)[C01]



- (b) State Norton's theorem. Find the current through  $10\Omega$  by using Norton's theorem for a given circuit shown in Fig.2. (7)[C01]


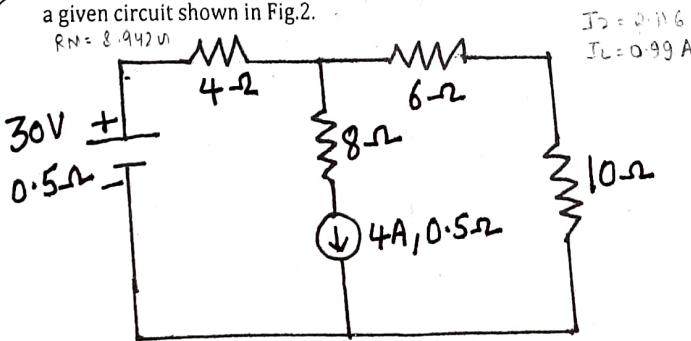


Fig.2

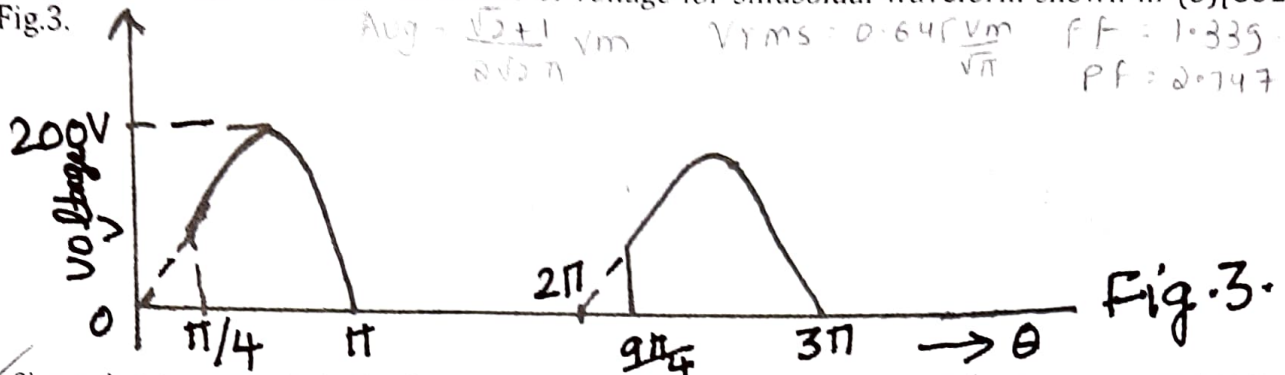- Q3 (a) Find the average and effective values of voltage for sinusoidal waveform shown in Fig.3. (5)[CO2]



- (b) Show that in a purely inductive circuit current lags the voltage by  $90^\circ$ . Also show that the average power consumed by it is always zero. (5)[CO2]

- (c) Draw resonance curve. Also define selectivity and Quality factor. (5)[CO2]

- Q4 (a) Discuss two-wattmeter method for power measurement in three-phase system feeding balanced load. Derive the expression for the power delivered and power factor. (8)[CO2]

- (b) A balanced three-phase star load impedance of  $(5-j10)$  ohms per phase and is supplied from a balanced three-phase 400V, 50Hz ac supply. Calculate the values for (i) line voltages (ii) phase voltages (iii) line currents (iv) phase currents (v) total power consumption and power factor. (7)[CO2]
- Handwritten calculations:
- $$400/\sqrt{3} \text{ V}$$
- $$400/\sqrt{3} \text{ V}$$
- $$20.679 \text{ A}$$

- Q5 (a) Explain that "The main flux in a transformer remains practically invariable under all conditions of load". (5)[CO3]

- (b) Define (i) Voltage regulation (ii) Efficiency and (iii) Eddy current and Hysteresis losses in case of transformer. (5)[CO3]

- (c) Explain the working principle of dc motor. (5)[CO3]

- Q6 (a) Explain why single-phase Induction Machine is not self-starting using the concept of double field revolving theory. (8)[CO3]

- (b) Explain with neat diagram the construction details of three-phase Synchronous Machine. (7)[CO3]

- Q7 Write short notes on the followings

- (a) Earthing

(5)[CO4]

- (b) Earth-Leakage Circuit Breaker (ELCB)

(5)[CO4]

- (c) Power factor improvement methods

(5)[CO4]

\*\*\*\*\*