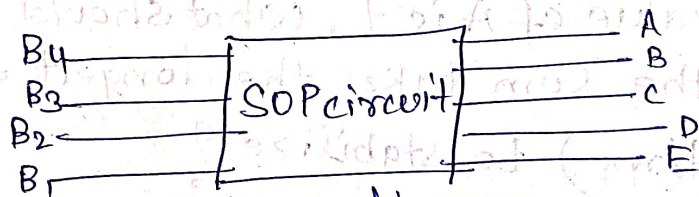


Q.1

Decimal	4 bit binary				BCD output				
	B <sub>4</sub>	B <sub>3</sub>	B <sub>2</sub>	B <sub>1</sub>	A	B	C	D	E
0	0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	0	1
2	0	0	1	0	0	0	0	1	0
3	0	0	1	1	0	0	0	1	1
4	0	1	0	0	0	0	1	0	0
5	0	1	0	1	0	0	1	0	1
6	0	1	1	0	0	0	1	1	0
7	0	1	1	1	0	0	1	1	1
8	1	0	0	0	0	1	0	0	0
9	1	0	0	1	0	1	0	0	1
10	1	0	1	0	1	0	0	0	0
11	1	0	1	1	1	0	0	0	1
12	1	1	0	0	1	0	0	1	0
13	1	1	0	1	1	0	0	1	1
14	1	1	1	0	1	0	1	0	0
15	1	1	1	1	1	0	1	0	1



b) block diagram

Ans 2 We consider the last full address for worst case delay

- Time after which output carry bit becomes available from the last full address.

= Total no of full address X carry propagation delay of full adder

= Total no of full address X { propagation delay of AND gate + propagation delay of OR gate }

=  $16 \times \{ 15 \text{ ns} + 10 \text{ ns} \}$

=  $16 \times 25 \text{ ns} = \boxed{400 \text{ ns}}$  Ans

- Time after which output sum bit becomes available (2)  
from the last full adder

= Time taken for its carry in to become available + Sum propagation delay of full adder

= { Total no of full adder before last full adder  $\times$  carry propagation delay of full adder } + propagation delay of XOR gate

$$= \{ 15 \times (15 \text{ ns} + 10 \text{ ns}) \} + 20 \text{ ns}$$

$$= \boxed{395 \text{ ns}}$$

Ans. 3 if the decimal value of A is 1, what should be the value of B, so that the sum takes the longest latency (i.e. the most time) to stabilize?

A = 1 (binary : 0000 0001)


- So to maximize latency, we want the carry to propagate through all 8 bits, from MSB to LSB.

So the full B = 1111 1111  $\rightarrow$  which is -1 in two's complement.

- In 2's complement, the MSB represents the sign : 0 for +ve and 1 for -ve.
- To find the decimal value of a negative number in 2's complement, you first need to find the 2's complement of the given number. Find the 2's complement of the binary number and then convert to decimal. If the original number's MSB was 1, add a -ve sign.



Ans. 4

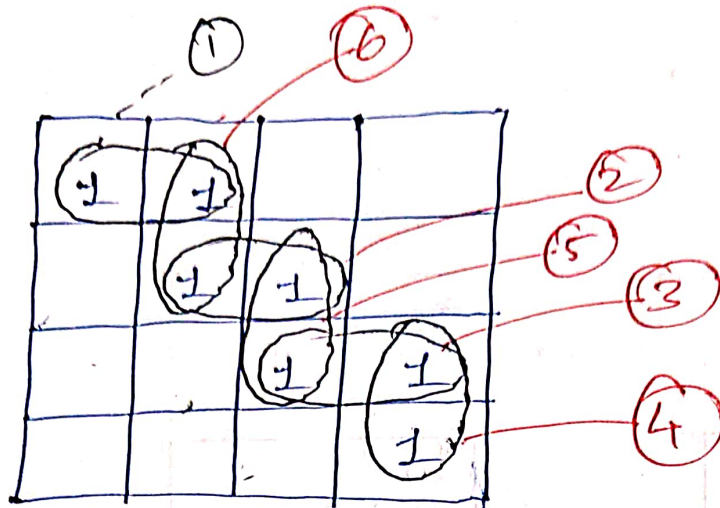

(3)

No of implicants = 7

PI = (1, 2, 3, 4, 5, 6)

EPI = (1, 4)

SPI = (2, 3, 5, 6)

$$F = \textcircled{1} + \textcircled{2} + \textcircled{3} + \textcircled{4}$$

OR

$$F = \textcircled{1} + \textcircled{5} + \textcircled{6} + \textcircled{4}$$

No of implicants = 7

No of prime implicants (PI) = 6

No of Essential (PI) = 2 (EPI)

No of Redundant PI = 2 (RPI)

No of Selective PI (SPI) = 4

Ans. 5


X	Y	Z <sub>n</sub>	D	Z <sub>n+1</sub>	J	K	Q <sub>n</sub>	Q <sub>n+1</sub>
0	0	0	0	0	0	0	0	0
0	0	1	1	1	0	0	1	1
0	1	0	1	1	0	1	0	0
0	1	1	1	1	0	1	1	0
1	0	0	0	0	1	0	0	1
1	0	1	0	0	1	0	1	1
1	1	0	1	1	1	1	0	1
1	1	1	0	0	1	1	1	0

$$X = K \text{ \& } Y = J$$

$$D = X'Z_n + YZ_n'$$


4

Ans. 6

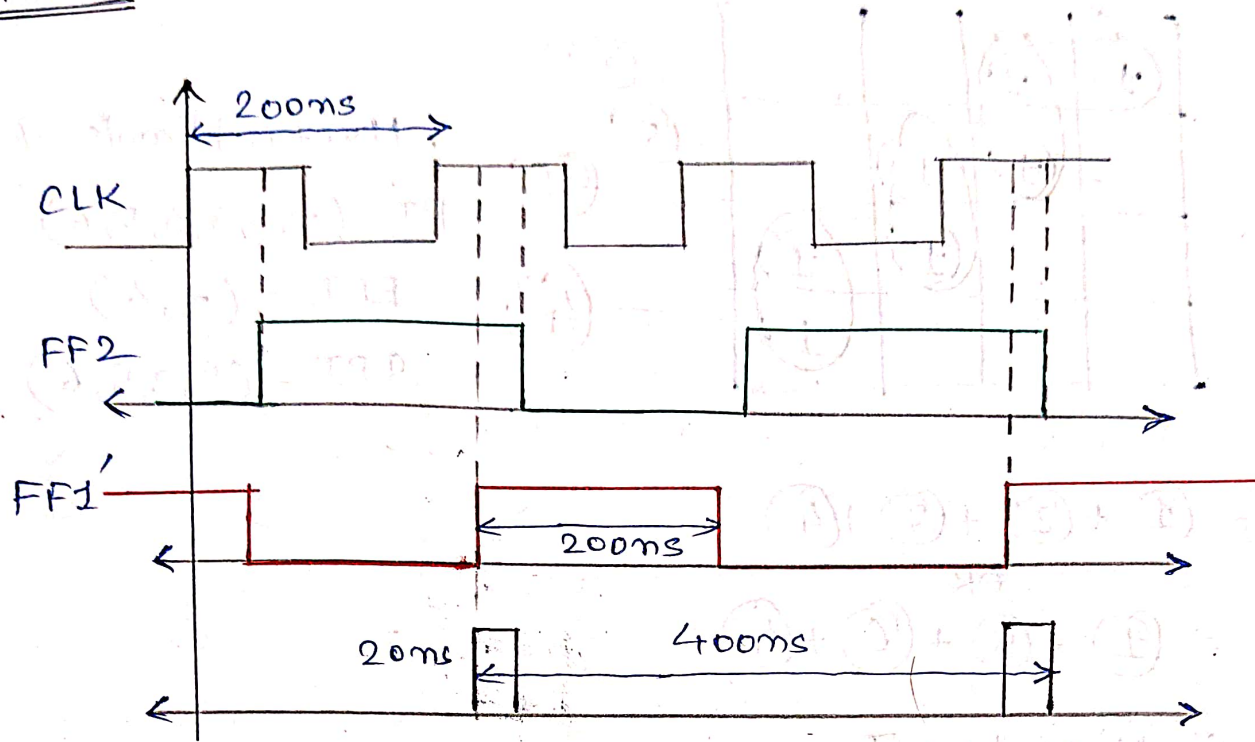

Duty cycle = 5%

Ans. 7

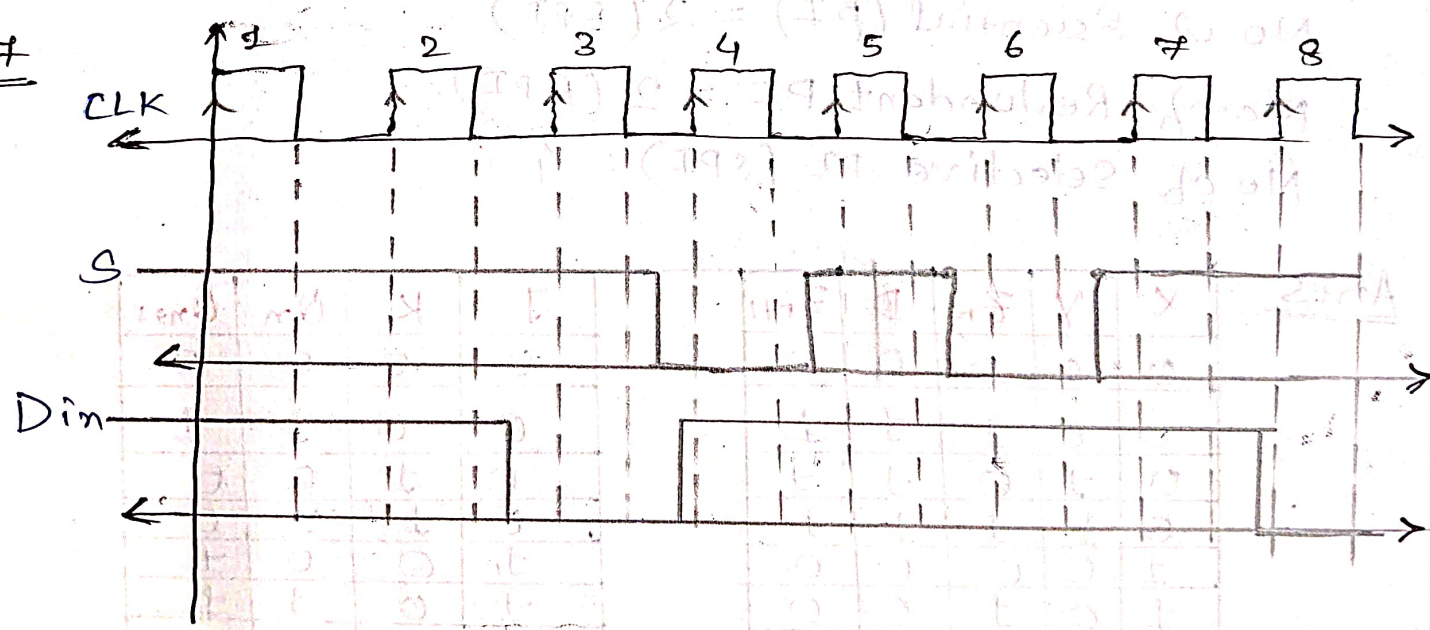

Ans. 7 (table)

$$Y = (Q_2' Q_1 Q_0)'$$

Signals			Inputs			Outputs			
CLK	D <sub>IN</sub>	S	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	Y
1	1	1	1	0	0	1	0	0	1
2	1	1	1	1	0	1	1	0	1
3	0	1	0	1	1	0	1	1	0
4	1	0	0	1	1	0	1	1	0
5	1	1	1	0	1	1	0	1	1
6	1	0							
7	1	1							
8	0	1							