
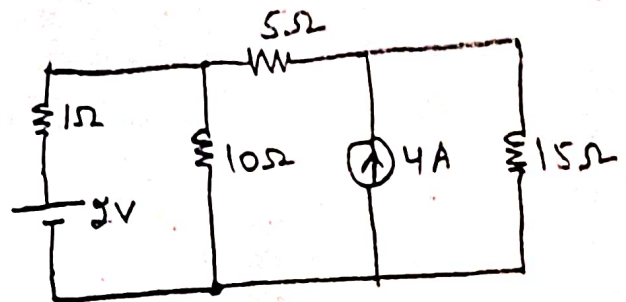


NATIONAL INSTITUTE OF TECHNOLOGY, KURUKSHETRA  
DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING  
SESSIONAL-I  
CIRCUIT THEORY (ECPC-101)



TIME: 45 MINS

MAX. MARKS: 20

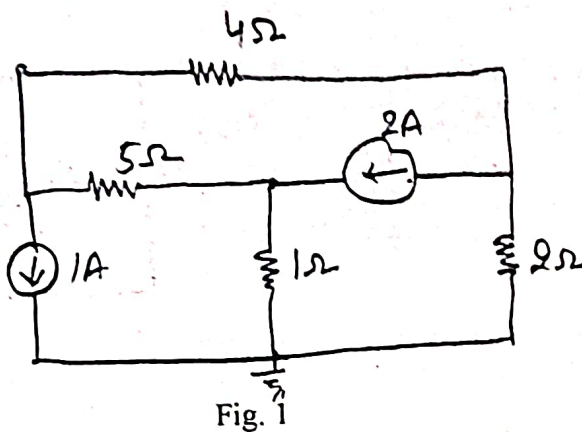1. Find the voltage drop across  $5\Omega$  resistor in the network shown in Fig. 1 using nodal analysis. 5 Marks



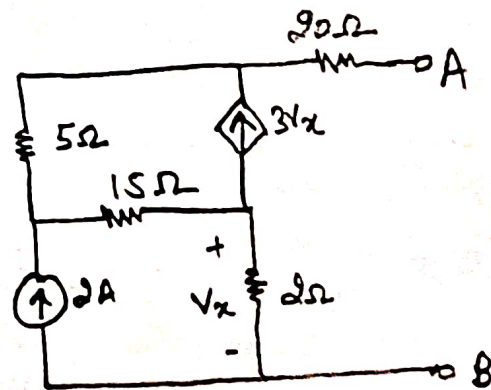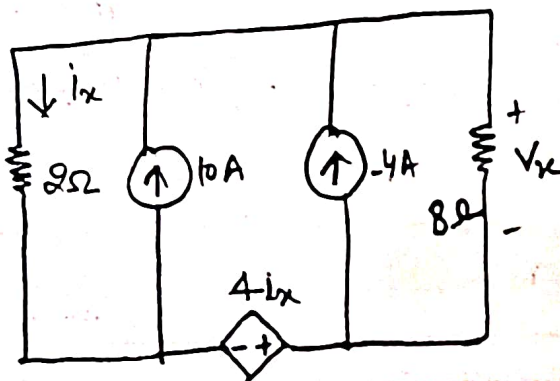2. In Fig. 2, find the current through  $10\Omega$  resistor using mesh analysis. 5 Marks  
3. In Fig. 3, find  $v_x$  using superposition theorem 5 Marks



4. Find the Norton's equivalent circuit across the terminals A-B in Fig. 4. 5 Marks