



Major Examination

Course Title: Fundamentals of Electrical and Electronics Engineering (EE101)


MM: 50

Duration: 3:00 Hrs


Note:

1. All parts of a question should be answered consecutively.
2. All the questions are compulsory.

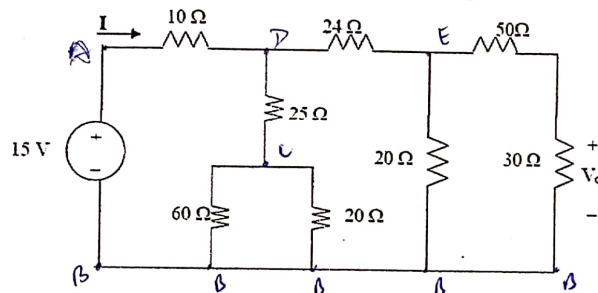
Q1. (a) Define Kirchoff's laws. Find I and v_o in the following circuit.



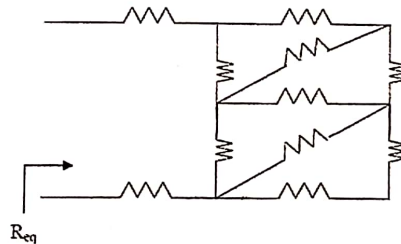(b) Derive the expression for transformation from a delta network to Y network and hence find the equivalent resistance of the following circuit where all resistors are of equal value of 1Ω .



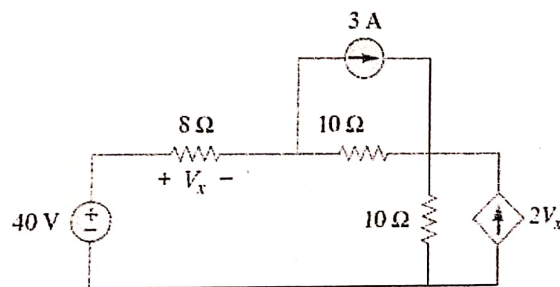
(c) Using source transformation, find the voltage v_x in the following circuit.



$$v_x = \frac{20}{47}$$


(d) Define maximum power transfer theorem and hence derive the condition for maximum power transfer across the load resistance of a given circuit.

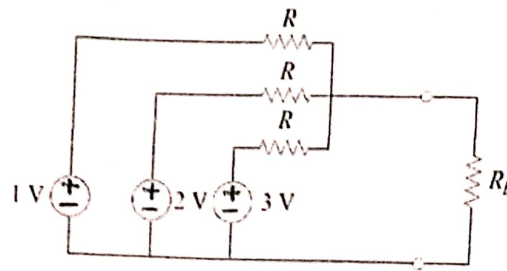- (c) For the circuit shown in figure below, determine the value of R such that the maximum power delivered to the load is 3 mW.




[2+3+2+3+3]

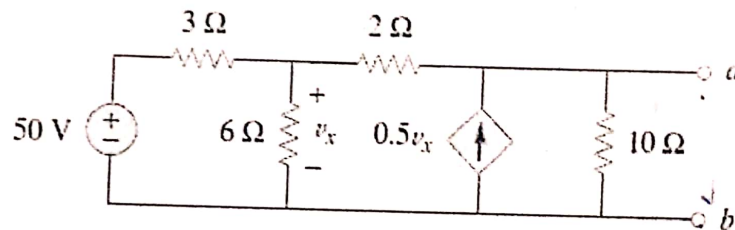
- Q.2. (a) Define Norton's theorem and hence prove the same.
(b) Obtain the Thevenin and Norton equivalent circuits at terminals a-b for the circuit shown below



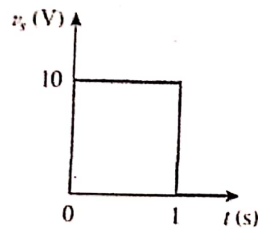- (c) If the input pulse in following figure (a) is applied to the circuit in figure (b), determine the response $i(t)$.




(a)

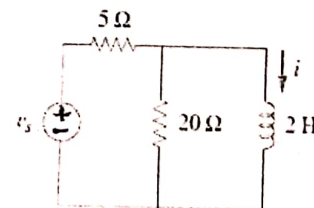

(b)

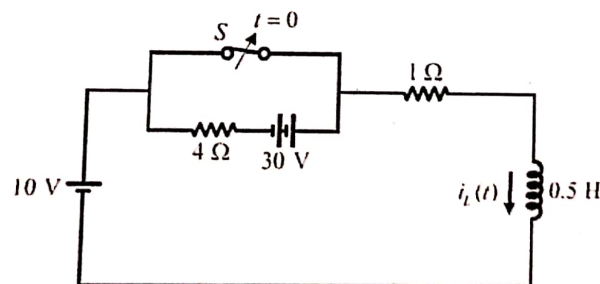- (d) In the circuit, switch 'S' is in the closed position for a very long time. If the switch is opened at time $t=0$, then find $i_L(t)$ in Amperes for $t \geq 0$.




[4+3+2.5+2.5]


3. (a) What is Hall effect? Briefly explain the significance of the same. Also derive the relationship of hall coefficient with mobility.

- (b) Briefly explain Zener and Avalanche breakdown highlighting the impact of temperature on the I-V characteristics curve. With a circuit diagram explain how Zener diode can be used as a voltage regulator.

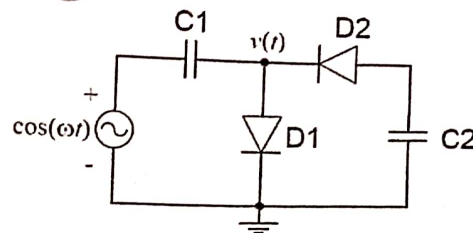- (c) The diodes and capacitors in the circuit shown are ideal. Find the voltage $v(t)$ across the diode D1? Also plot the input and output voltage waveform.




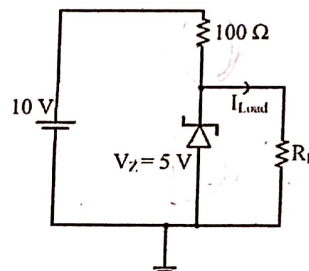- (d) In the circuit shown below, the knee current of the ideal Zener diode is 10 mA. To maintain 5 V across R_L , find the minimum value of R_L in Ω and the minimum power rating of the Zener diode in mW.



[4+3+3+3]

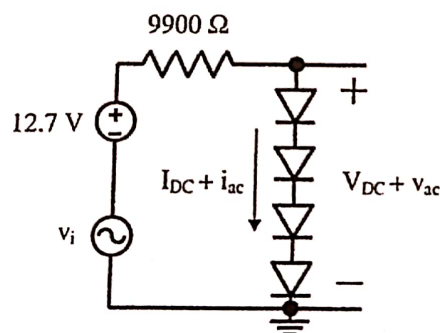4. (a) With a neat diagram briefly explain the distribution of charge, electric field intensity, potential barrier across an open circuit p-n junction. Hence explain the use of same as a rectifier.
 (b) What is the significance of piecewise linear model of a diode. Draw piecewise linear equivalent circuit of a diode.
 (c) A silicon PN junction is forward biased with a constant current at room temperature. When the temperature is increased by 10°C , what would be the reduction in forward bias voltage across the PN junction?
 (d) In the circuit shown below, assume that the voltage drop across a forward biased diode is 0.7 V. The thermal voltage $V_t = \frac{KT}{q} = 25\text{ mV}$. The small signal input $v_i = v_p \cos(\omega t)$ where $v_p = 100\text{ mV}$. Then find the bias current I_{DC} through the diodes and ac output voltage.



[4+2+2+4]