



WALCHAND COLLEGE OF ENGINEERING

(Government Aided Autonomous Institute)

Vishnambag, Sangli - 416415

First Year B.Tech. Group B (Civil, Mech, ELE)

ESE, ODD SEMESTER, AY 2022-23

Basic Electrical Engineering (6EL101)



ESE

PRN: _____

Day & Date: Friday, 03/03/2023

Time: 10.30 am to 12.30 pm

Max Marks: **50**

IMP: Verify that you have received question papers with correct course code, branch etc.


- Instructions**
- a) All questions are compulsory.
 - b) Writing question number on answer book is compulsory otherwise answers may not be assessed.
 - c) Assume suitable data wherever necessary.
 - d) Figures to the right of question text indicate full marks.
 - e) Mobile phones, smart gadgets and programmable calculators are strictly prohibited.
 - f) Except PRN anything else writing on question paper is not allowed.
 - g) Exchange/Sharing of stationery, calculator etc. not allowed.

Text on the right of marks indicates course outcomes (Only for faculty use)

Marks

Q1 A) Find out the current flowing through $200\ \Omega$ resistor with proper direction.

5 CO2

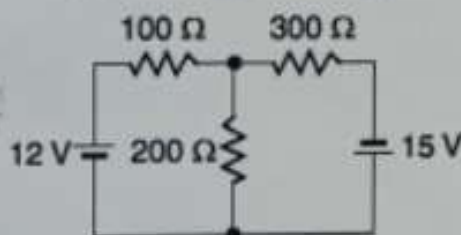

B) What is meant by "Leading" & "Lagging" in AC Circuits. A resistance of $140\ \Omega$, inductance of $0.85\ \text{H}$ & Voltage Source of $120\ \text{V}$ (RMS Value), $60\ \text{Hz}$ are connected in series. Determine the Current in the circuit, the p.f. of the circuit.

6 CO2

Q2 A) Derive EMF equation of DC Motor. An 8-pole lap connected armature has 960 conductors, a flux per pole of $40\ \text{mWb}$. & a speed of $400\ \text{rpm}$. Determine the EMF generated.

8 CO2

B) A $100/400\ \text{V}$ Transformer is connected with $100\ \text{ohm}$ load on secondary side. Calculate Primary Side Current, Secondary Side Current & Equivalent Impedance referred to Primary Side.

5 CO2

Q3 A) Describe working principle of Single Phase Transformer with proper diagram. Also write the induced EMF equations on Primary & Secondary Side.

6 CO1

- B) State what is Synchronous Speed & Slip. Explain any 1 type of starting method of 1 Phase Induction Motor. For a three-phase, 4-pole, 50-Hz induction motor, find out the Synchronous Speed. Also find out Rotor Speed at slip of 4 %.

Q4 A) Describe what is a Fuse and also its necessity. List different types of fuses.

OR

List out different types of electric lamp. Describe any one lamp in detail

- B) State different types of wires. Draw the general construction diagram of Cable with proper labeling.

.....End of question paper