



(Please write your Enrollment Number)



Enrollment No. _____

End-Term Examination
(CBCS)(SUBJECTIVE TYPE)(OffLine)
B.Tech:<>, III Semester:<>
(December, 2024)

Subject Code: BEC 205	Subject: Network Analysis and Synthesis
Time :3 Hours	Maximum Marks :60

Note: Q1 is compulsory. Attempt one question each from the Units I, II, III & IV.

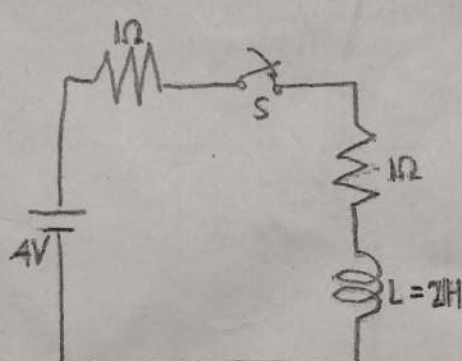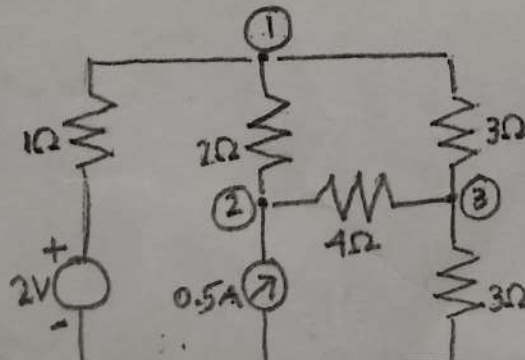Q1	(2.5*8=20)	CO Mapping
a) What is source transformation technique? Explain by transforming a voltage source to a current source and vice versa.		CO1
b) Explain KCL and KVL.		CO1
c) In the circuit shown in Figure, the switch s is closed at $t=0$ then determine the steady state value of the current.		CO2
		
d) What do you understand by time constant of a circuit?		CO1
e) If $Z = (4+j6)$ Ohm then find the value of Conductance G and Susceptance B ?		CO2
f) Derive the condition of symmetry in terms of Z -parameters		CO2
g) What do you understand by positive real function?		CO1
h) What are the necessary conditions for driving point functions?		CO1
UNIT I		CO Mapping
Q2	Prove that maximum power is delivered from a source having internal impedance Z_s , to a connected load impedance Z_L , when $Z_L = Z_s^*$.	(10) CO2
Q3	Using nodal analysis, find the power dissipated in the 4 ohm resistor of the network shown in Figure.	(10) CO3
		

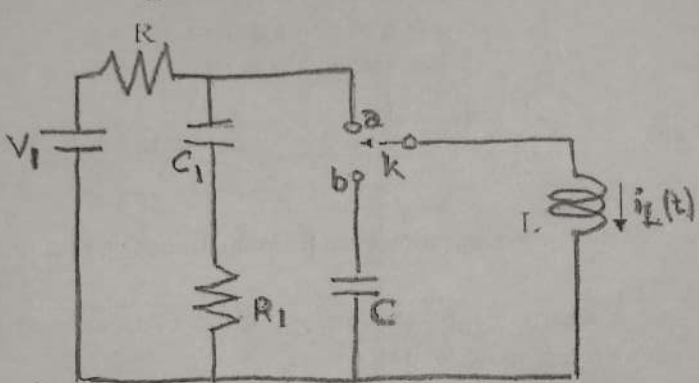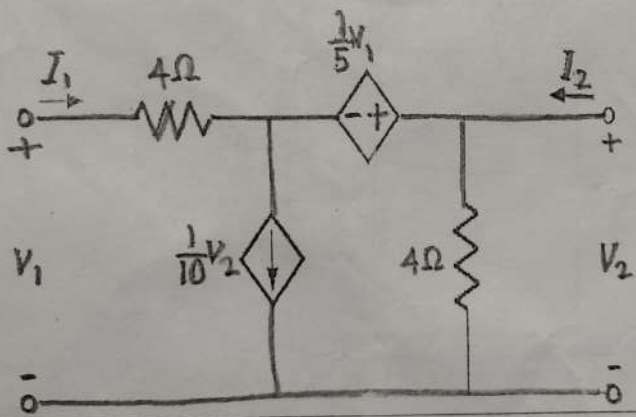UNIT II		CO Mapping
Q4	<p>The switch K, as shown in the Fig.4 is in steady state position 'a' for $t < 0$. At $t = 0$, it is shifted to position 'b'. Find $i_L(t)$, for $t \geq 0$.</p> 	(10) CO3
Q5	What is graph theory? Explain its applications with one example.	(10) CO3
UNIT III		CO Mapping
Q6	Find T parameters of the circuit shown in figure below:	(10) CO4
		
Q7	What do you understand by h-parameters? Derive h-parameters for a two port network and clearly explain the procedure. Draw the equivalent circuit model.	(10) CO2
UNIT IV		CO Mapping
Q8	Explain concept of poles & zeroes. Discuss restrictions on pole and zero locations for driving point functions.	(10) CO2
Q9	<p>Synthesize a network using Foster-I and Foster -II forms for the impedance function:</p> $Z(s) = \frac{s(s^2 + 9)}{(s^2 + 5)(s^2 + 13)}$	(10) CO4